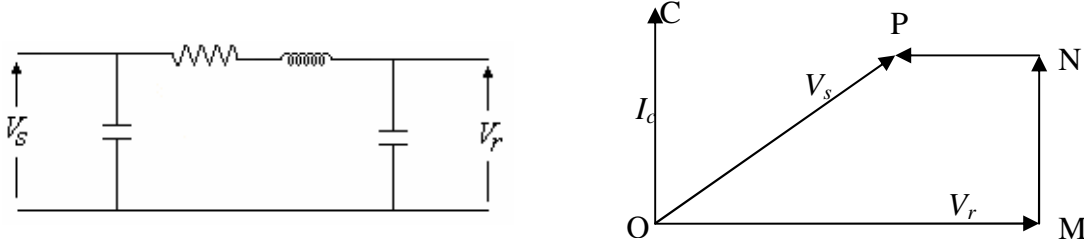


# Ferranti Effect

A long transmission line draws a substantial quantity of charging current. If such a line is open circuited or very lightly loaded at the receiving end, the voltage at receiving end may become greater than voltage at sending end. This is known as **Ferranti Effect** and is due to the voltage drop across the line inductance (*due to charging current*) being in phase with the sending end voltages. Therefore both capacitance and inductance is responsible to produce this phenomenon.

The capacitance (*and charging current*) is negligible in short line but significant in medium line and appreciable in long line. Therefore this phenomenon occurs in medium and long lines.

Represent line by equivalent  $\pi$ -model.



Line capacitance is assumed to be concentrated at the receiving end.

OM = receiving end voltage  $V_r$

OC = Current drawn by capacitance =  $I_c$

MN = Resistance drop

NP = Inductive reactance drop

Therefore;

OP = Sending end voltage at no load and is less than receiving end voltage ( $V_r$ )

Since, resistance is small compared to reactance; resistance can be neglected in calculating Ferranti effect.

From  $\pi$ -model,

$$V_s = \left(1 + \frac{YZ}{2}\right)V_r + ZI_r \quad \{\text{refer eq. 5, in } \pi\text{-model ckt. derivation}\}$$

For open circuit line;  $I_r = 0$

$$\therefore V_s = \left(1 + \frac{YZ}{2}\right)V_r$$

$$\text{or; } V_s - V_r = \left(1 + \frac{YZ}{2}\right)V_r - V_r = V_r \left(1 + \frac{YZ}{2} - 1\right)$$

$$\text{or; } V_s - V_r = \left(\frac{YZ}{2}\right)V_r = \frac{(j\omega Cl)(r + j\omega L)l}{2} V_r$$

Neglecting resistance;

$$V_s - V_r = \frac{-V_r \omega^2 l^2 LC}{2}$$

The quantity  $\frac{1}{\sqrt{LC}}$  is constant in all line and is equal to velocity of propagation of electromagnetic waves ( $= 3 \times 10^5$  km/sec)

$$\sqrt{LC} = \frac{1}{(3 \times 10^5)} \Rightarrow LC = \frac{1}{(3 \times 10^5)^2}$$

Substituting the value in above equation;

$$V_s - V_r = \frac{-V_r \omega^2 l^2}{2(3 \times 10^5)^2}$$

$$\therefore V_s - V_r = \frac{-V_r \omega^2 l^2 \times 10^{-10}}{18}$$

$$\boxed{\therefore V_s = V_r \left[ 1 - \frac{\omega^2 l^2 \times 10^{-10}}{18} \right]}$$

Now, from above expression;

$$\left[ 1 - \frac{\omega^2 l^2 \times 10^{-10}}{18} \right] < 1$$

So,

$$V_s < V_r \quad \text{or;} \quad V_r > V_s$$

i.e. receiving end voltage is greater than sending end voltage and this effect is called Ferranti Effect. It is valid for open circuit condition of long line.